

Computer Architecture


ECE 361

Lecture 6: ALU Design

361 ALU.1

Review: ALU Design

 - Bit-slice plus extra on the two ends
- Overflow means number too large for the representation
- Carry-look ahead and other adder tricks



361 ALU.2

Review: Elements of the Design Process

- **Divide and Conquer (e.g., ALU)**
 - **Formulate** a solution in terms of simpler components.
 - **Design** each of the components (subproblems)
- **Generate and Test (e.g., ALU)**
 - **Given** a collection of building blocks, look for ways of putting them together that meets requirement
- **Successive Refinement (e.g., multiplier, divider)**
 - **Solve "most"** of the problem (i.e., ignore some constraints or special cases), examine and correct shortcomings.
- **Formulate High-Level Alternatives (e.g., shifter)**
 - **Articulate** many strategies to "keep in mind" while pursuing any one approach.
- **Work on the Things you Know How to Do**
 - The unknown will become "obvious" as you make progress.

361 ALU.3

Outline of Today's Lecture

- **Deriving the ALU from the Instruction Set**
- **Multiply**

361 ALU.4

MIPS arithmetic instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comments</i>
add	add \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; exception possible
add immediate	addi \$1,\$2,100	$\$1 = \$2 + 100$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; no exceptions
add imm. unsign. constant; no exceptions	addiu \$1,\$2,100	$\$1 = \$2 + 100$	+
multiply	mult \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit unsigned product
divide	div \$2,\$3	Lo = $\$2 \div \3 ,	Lo = quotient, Hi = remainder
			Hi = $\$2 \bmod \3
divide unsigned remainder	divu \$2,\$3	Lo = $\$2 \div \3 ,	Unsigned quotient &
			Hi = $\$2 \bmod \3
Move from Hi	mfhi \$1	$\$1 = \text{Hi}$	Used to get copy of Hi
Move from Lo	mflo \$1	$\$1 = \text{Lo}$	Used to get copy of Lo

361 ALU.5

MIPS logical instructions

<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \mid \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \mid \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 \mid 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \sim\$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable

361 ALU.6


Additional MIPS ALU requirements

- Xor, Nor, Xorl
=> Logical XOR, logical NOR or use 2 steps: $(A \text{ OR } B) \text{ XOR } 1111\dots1111$
- Sll, Srl, Sra
=> Need left shift, right shift, right shift arithmetic by 0 to 31 bits
- Mult, MultU, Div, DivU
=> Need 32-bit multiply and divide, signed and unsigned

361 ALU.7

Add XOR to ALU

- Expand Multiplexor

 

361 ALU.8


Shifters

Three different kinds:

logical-- value shifted in is always "0"



 arithmetic-- on right shifts, sign extend



rotating-- shifted out bits are wrapped around (not in MIPS)



Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Administrative Matters

MULTIPLY (unsigned)


- Paper and pencil example (unsigned):

Multiplicand	1000	
Multiplier	1001	
		1000
		0000
		0000
		1000
Product	01001000	

- $m \text{ bits} \times n \text{ bits} = m+n \text{ bit product}$
- Binary makes it easy:
 - 0 $\Rightarrow$ place 0 (0 x multiplicand)
 - 1 $\Rightarrow$ place a copy (1 x multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement

361 ALU.11


Unsigned Combinational Multiplier

 

- Stage i accumulates $A * 2^i$ if $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?

361 ALU.12

How does it work?

 


- ° at each stage shift A left ($\times 2$)
- ° use next bit of B to determine whether to add in shifted multiplicand
- ° accumulate 2n bit partial product at each stage

361 ALU.13

Unsigned shift-add multiplier (version 1)

 
- ° 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control

361 ALU.14

Multiply Algorithm Version 1

 


Observations on Multiply Version 1

- ° 1 clock per cycle => - 100 clocks per multiply
 - Ratio of multiply to add 5:1 to 100:1
- ° 1/2 bits in multiplicand always 0
=> 64-bit adder is wasted
- ° 0's inserted in left of multiplicand as shifted
=> least significant bits of product never changed once formed
- ° Instead of shifting multiplicand to left, shift product to right?


MULTIPLY HARDWARE Version 2

 - 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg




361 ALU.17

Multiply Algorithm Version 2

 

361 ALU.18


What's going on?

 

- Multiplicand stay's still and product moves right

361 ALU.19

Multiply Algorithm Version 2

 

361 ALU.20


Observations on Multiply Version 2

- ° Product register wastes space that exactly matches size of multiplier
=> combine Multiplier register and Product register


361 ALU.21

MULTIPLY HARDWARE Version 3

 - ° 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



361 ALU.22

 

Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU
- How can you make it faster?
- What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - apply definition of 2's complement
 - need to sign-extend partial products and subtract at the end
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can handle multiple bits at a time

Motivation for Booth's Algorithm

- Example $2 \times 6 = 0010 \times 0110$:

0010	
x 0110	
+ 0000	shift (0 in multiplier)
+ 0010	add (1 in multiplier)
+ 0100	add (1 in multiplier)
+ 0000	shift (0 in multiplier)
00001100	

- ALU with add or subtract gets same result in more than one way:


$$\begin{array}{lcl}
 6 & = & -2 + 8 \\
 0110 & = & -0010 + 1000
 \end{array}
 , \text{ or }$$

- Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one. For example

0010	
x 0110	
+ 0000	shift (0 in multiplier)
- 0010	sub (first 1 in multiplier)
+ 0000	shift (middle of string of 1s)
+ 0010	add (prior step had last 1)
00001100	

361 ALU.25

Booth's Algorithm Insight

 

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	000111 <u>1</u> 000
0	1	End of a run of 1s	000 <u>1</u> 111000
0	0	Middle of a run of 0s	<u>0</u> 001111000

Originally for Speed since shift faster than add for his machine

Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one

361 ALU.26

Booths Example (2 x 7)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 0111 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 0111 0	shift P (sign ext)
1b.	0010	1111 0011 1	11 -> nop, shift
2.	0010	1111 1001 1	11 -> nop, shift
3.	0010	1111 1100 1	01 -> add
4a.	0010	+ 0010 0001 1100 1	shift
4b.	0010	0000 1110 0	done

361 ALU.27

Booths Example (2 x -3)

Operation	Multiplicand	Product	next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 1101 0	shift P (sign ext)
1b.	0010	1111 0110 1 + 0010	01 -> add
2a.		0001 0110 1	shift P
2b.	0010	0000 1011 0 + 1110	10 -> sub
3a.	0010	1110 1011 0	shift
3b.	0010	1111 0101 1	11 -> nop
4a		1111 0101 1	shift
4b.	0010	1111 1010 1	done

361 ALU.28

Booth's Algorithm

1. Depending on the current and previous bits, do one of the following:
 - 00: a. Middle of a string of 0s, so no arithmetic operations.
 - 01: b. End of a string of 1s, so add the multiplicand to the left half of the product.
 - 10: c. Beginning of a string of 1s, so subtract the multiplicand from the left half of the product.
 - 11: d. Middle of a string of 1s, so no arithmetic operation.
2. As in the previous algorithm, shift the Product register right (arith) 1 bit.

361 ALU.29

MIPS logical instructions


<i>Instruction</i>	<i>Example</i>	<i>Meaning</i>	<i>Comment</i>
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \mid \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \mid \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 \mid 10$	Logical OR reg, constant
xor immediate	xori \$1, \$2,10	$\$1 = \sim \$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2, \$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable

361 ALU.30


Shifters

Two kinds:

logical-- value shifted in is always "0"

 

 arithmetic-- on right shifts, sign extend




Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!


361 ALU.31

Combinational Shifter from MUXes

Basic Building Block

 


8-bit right shifter

 

- What comes in the MSBs?
- How many levels for 32-bit shifter?
- What if we use 4-1 Muxes ?

361 ALU.32

 General Shift Right Scheme using 16 bit example



If added Right-to-left connections could support Rotate (not in MIPS but found in ISAs)

361 ALU.33

Summary

- Instruction Set drives the ALU design
- Multiply: successive refinement to see final design
 - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
 - Booth's algorithm to handle signed multiplies
- There are algorithms that calculate many bits of multiply per cycle (see exercises 4.36 to 4.39)
- What's Missing from MIPS is Divide & Floating Point Arithmetic

361 ALU.34