

ECE 361
Computer Architecture
Lecture 11: Designing a Multiple Cycle Controller

361 multicontroller.1


Review of a Multiple Cycle Implementation

- The root of the single cycle processor's problems:
 - The cycle time has to be long enough for the slowest instruction
- Solution:
 - Break the instruction into smaller steps
 - Execute each step (instead of the entire instruction) in one cycle
 - Cycle time: time it takes to execute the longest step
 - Keep all the steps to have similar length
 - This is the essence of the multiple cycle processor
- The advantages of the multiple cycle processor:
 - Cycle time is much shorter
 - Different instructions take different number of cycles to complete
 - Load takes five cycles
 - Jump only takes three cycles
 - Allows a functional unit to be used more than once per instruction

361 multicontroller.2

Review: Instruction Fetch Cycle, In the Beginning

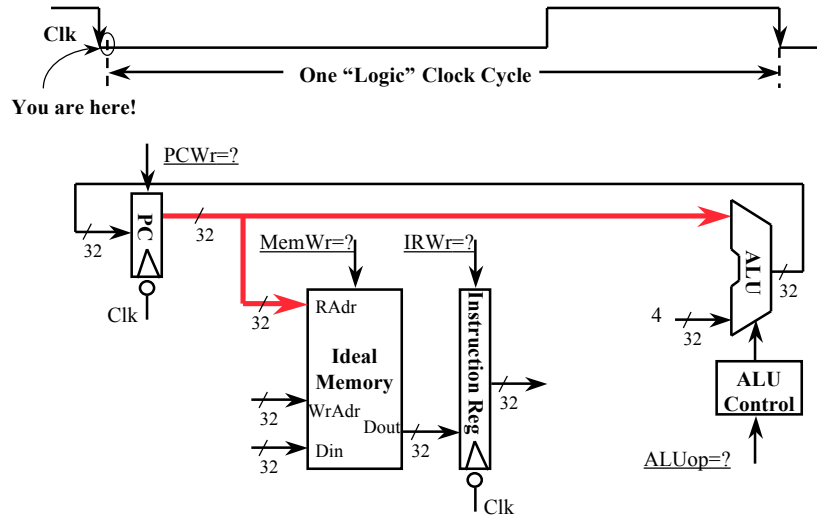
- Every cycle begins right AFTER the clock tick:
 - `mem[PC]` `PC<31:0> + 4`



361 multicontroller.3


Review: Instruction Fetch Cycle, The End

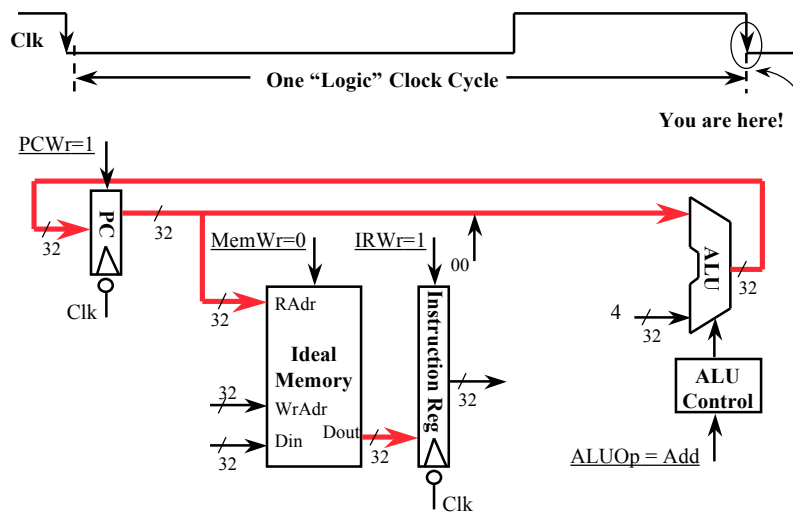- Every cycle ends AT the next clock tick (storage element updates):
 - $IR \leftarrow mem[PC]$ $PC[31:0] \leftarrow PC[31:0] + 4$




361 multicontroller.4

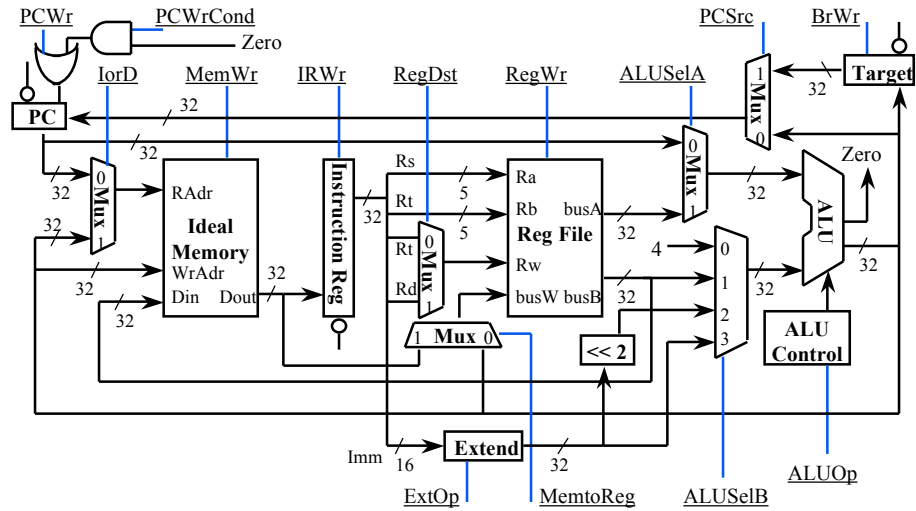Putting it all together: Multiple Cycle Datapath



Instruction Fetch Cycle: Overall Picture

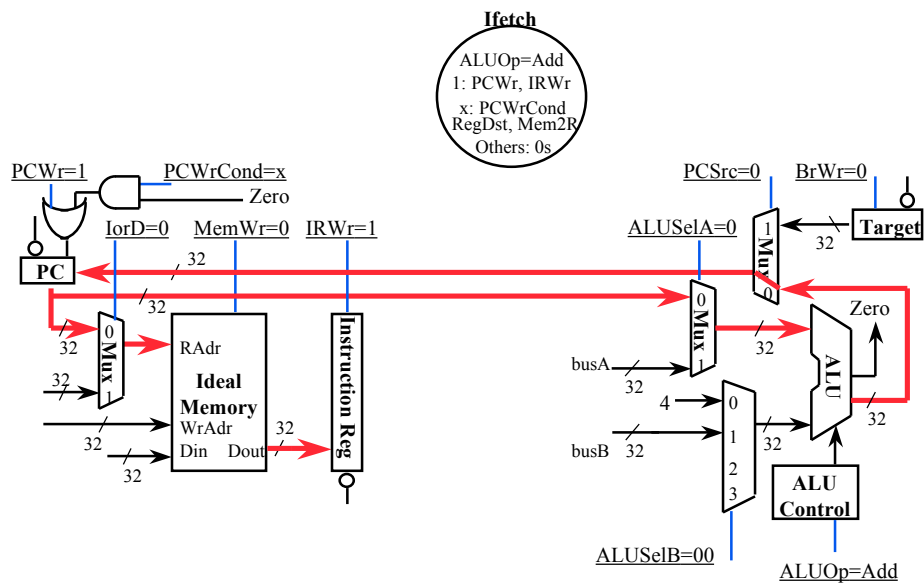


Register Fetch / Instruction Decode (Continue)

- ° $\text{busA} \leftarrow \text{Reg}[\text{rs}] ; \text{busB} \leftarrow \text{Reg}[\text{rt}] ;$
- ° $\text{Target} \leftarrow \text{PC} + \text{SignExt}(\text{Imm16}) * 4$

Rfetch/Decode

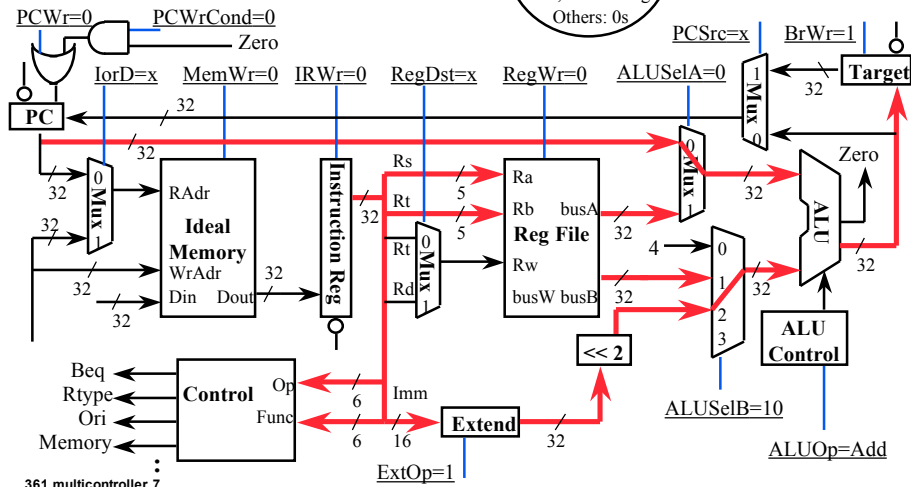ALUOp=Add
1: BrWr, ExtOp
ALUSelB=10
x: RegDst, PCSrc
IorD, MemtoReg
Others: 0s




361 multicontroller.7

R-type Execution

- ° $\text{ALU Output} \leftarrow \text{busA op busB}$

RExec

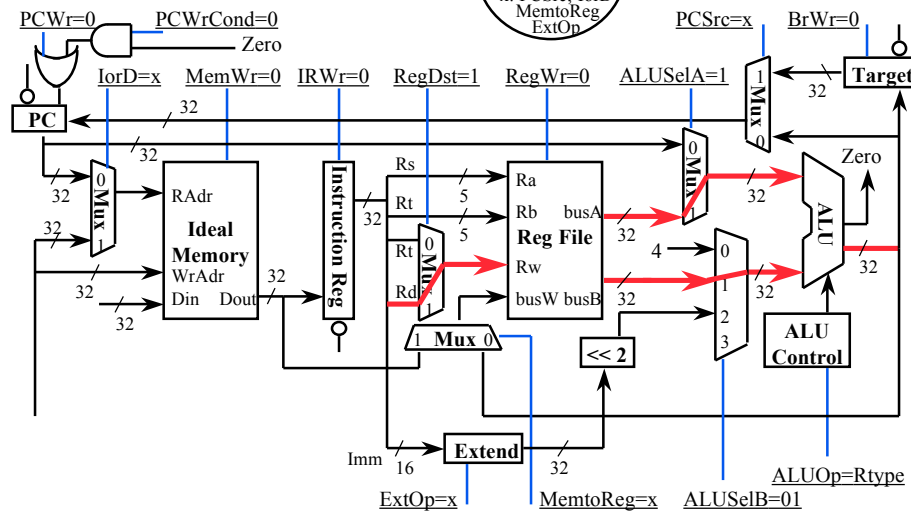
1: RegDst
ALUSelA
ALUSelB=01
ALUOp=Rtype
x: PCSrc, IorD
MemtoReg
ExtOp



361 multicontroller.8


Overview

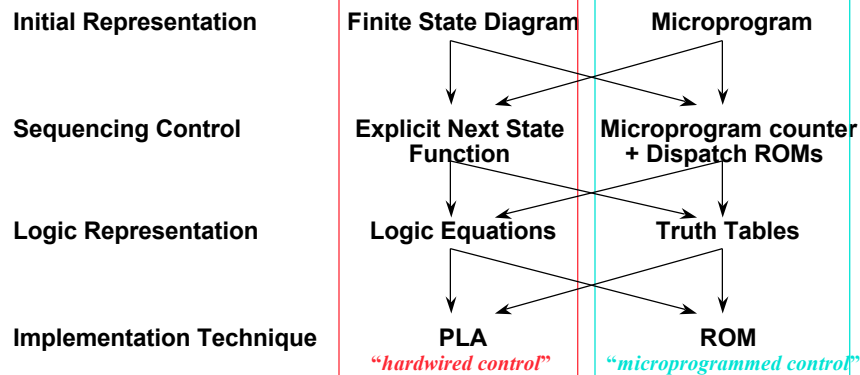- Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.




361 multicontroller.11

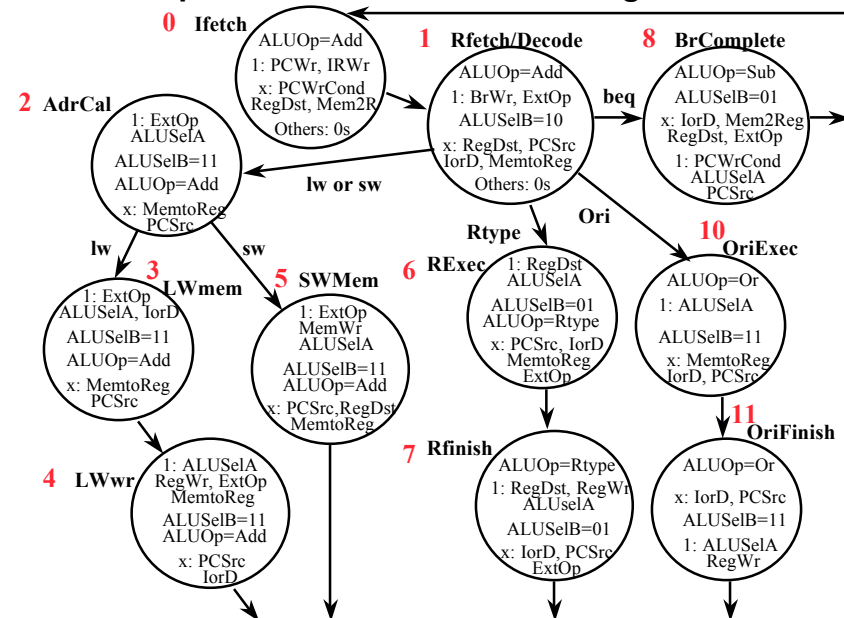Initial Representation: Finite State Diagram



361 multicontroller.12

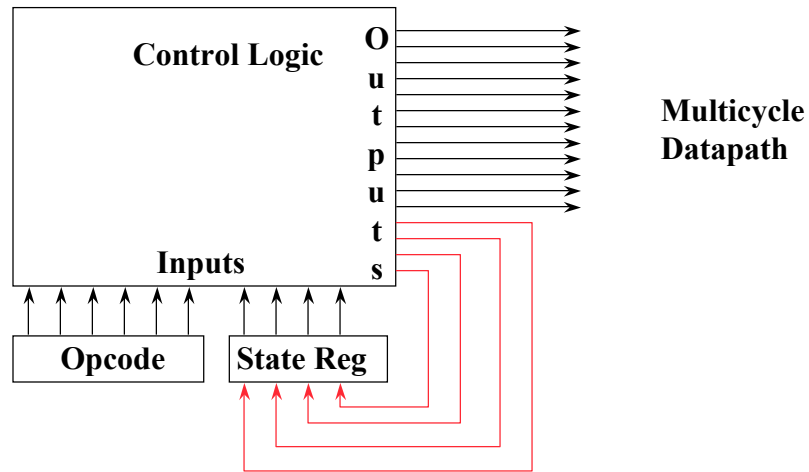Sequencing Control: Explicit Next State Function



- Next state number is encoded just like datapath controls

361 multicontroller.13


Logic Representative: Logic Equations

- Next state from current state
 - State 0 -> State1
 - State 1 -> S2, S6, S8, S10
 - State 2 -> _____
 - State 3 -> _____
 - State 4 -> State 0
 - State 5 -> State 0
 - State 6 -> State 7
 - State 7 -> State 0
 - State 8 -> State 0
 - State 9 -> State 0
 - State 10 -> State 11
 - State 11 -> State 0
- Alternatively, prior state & condition
 - S4, S5, S7, S8, S9, S11 -> State0
 - _____ -> State 1
 - _____ -> State 2
 - _____ -> State 3
 - _____ -> State 4
 - State2 & op = sw -> State 5
 - _____ -> State 6
 - State 6 -> State 7
 - _____ -> State 8
 - State2 & op = jmp -> State 9
 - _____ -> State 10
 - State 10 -> State 11

361 multicontroller.14


Implementation Technique: Programmed Logic Arrays

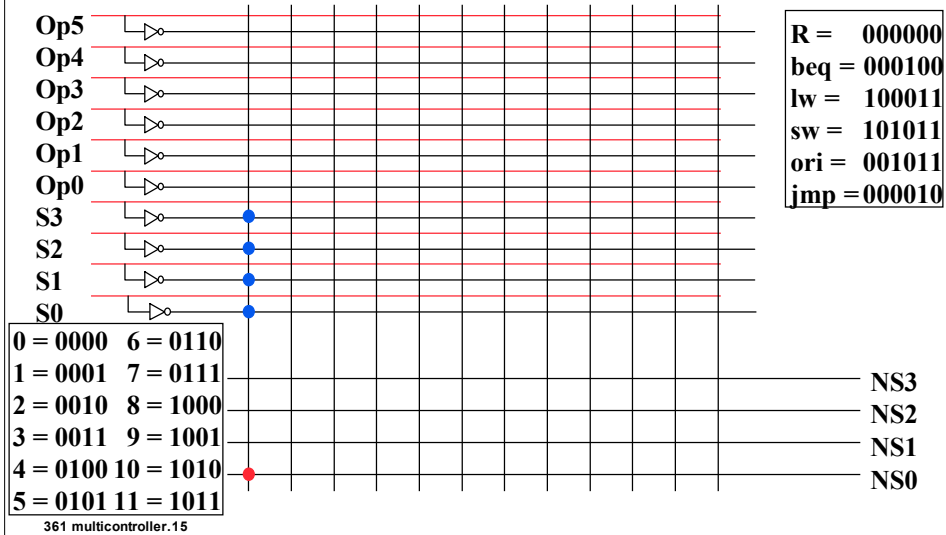- Each output line the logical OR of logical AND of input lines or their complement: AND minterms specified in top AND plane, OR sums specified in bottom OR plane



Implementation Technique: Programmed Logic Arrays

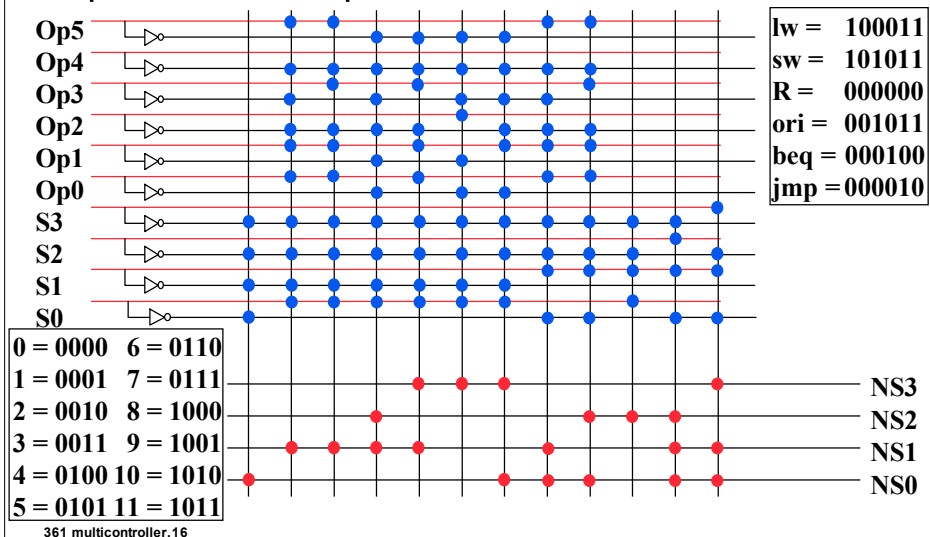- Each output line the logical OR of logical AND of input lines or their complement: AND minterms specified in top AND plane, OR sums specified in bottom OR plane




Multicycle Control

- Given numbers of FSM, can turn determine next state as function of inputs, including current state
- Turn these into Boolean equations for each bit of the next state lines
- Can implement easily using PLA
- What if many more states, many more conditions?
- What if need to add a state?



361 multicontroller.17

Next Iteration: Using Sequencer for Next State

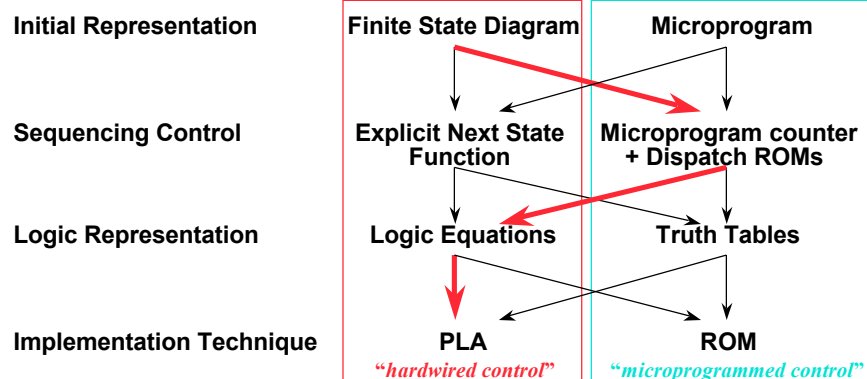- Before Explicit Next State: Next try variation 1 step from right hand side
- Few sequential states in small FSM: suppose added floating point?
- Still need to go to non-sequential states: e.g., state 1 => 2, 6, 8, 10



361 multicontroller.18

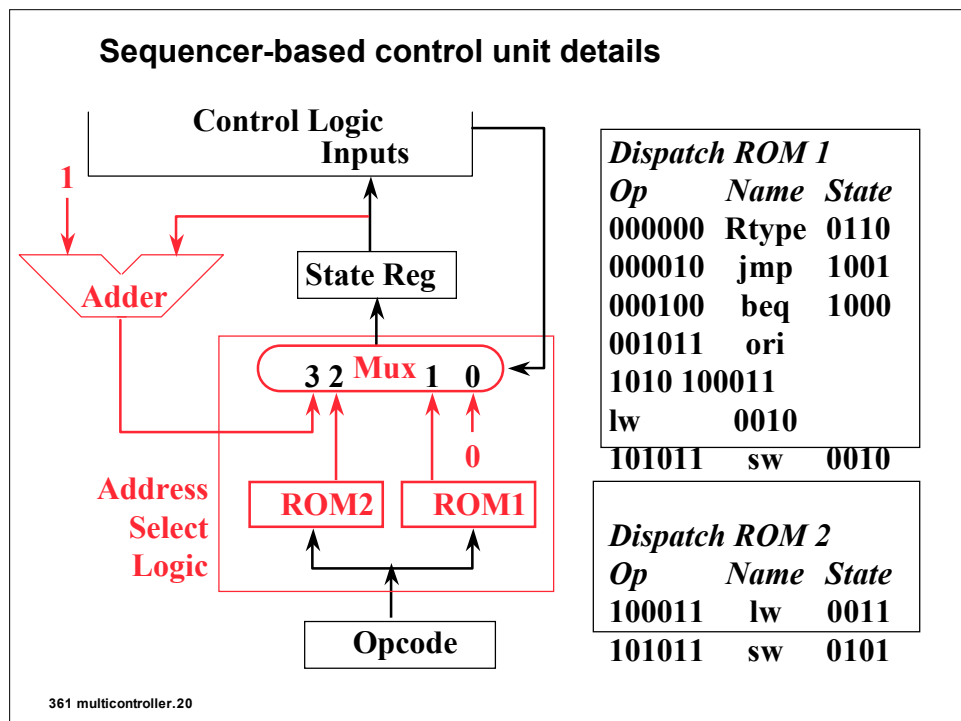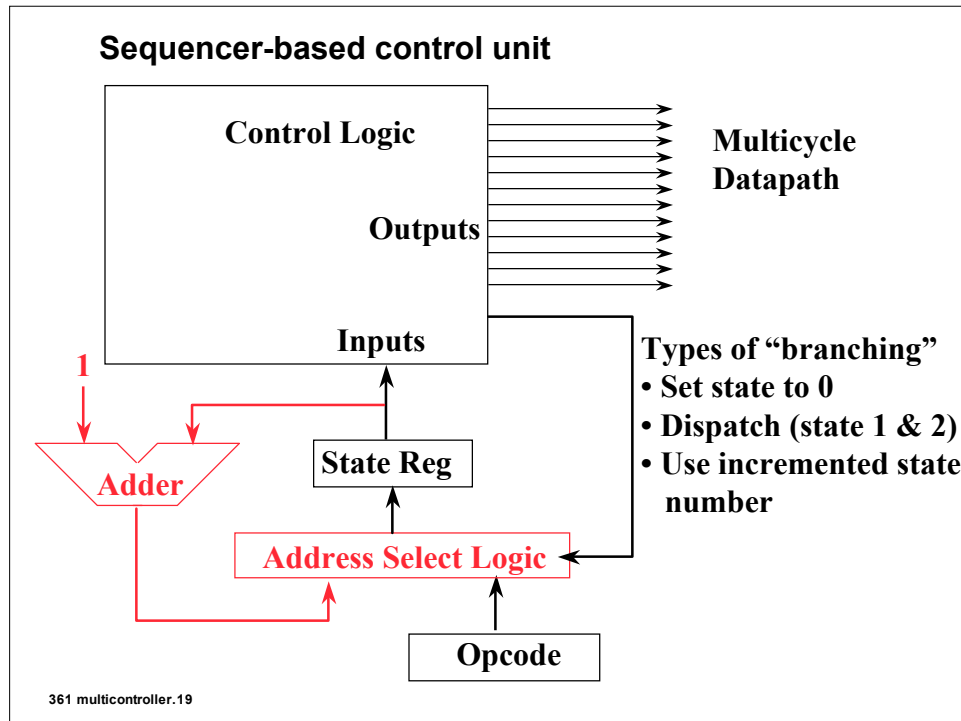


Implementing Control with a ROM

- ° Instead of a PLA, use a ROM with one word per state (“Control word”)

State number	Control Word Bits 18-2	Control Word Bits 1-0
0	10010100000001000	11
1	00000000010011000	01
2	00000000000010100	10
3	00110000000010100	11
4	00110010000010110	00
5	00101000000010100	00
6	00000000001000100	11
7	00000000001000111	00
8	01000000100100100	00
9	10000001000000000	00
10	...	11
11	...	00

361 multicontroller.21

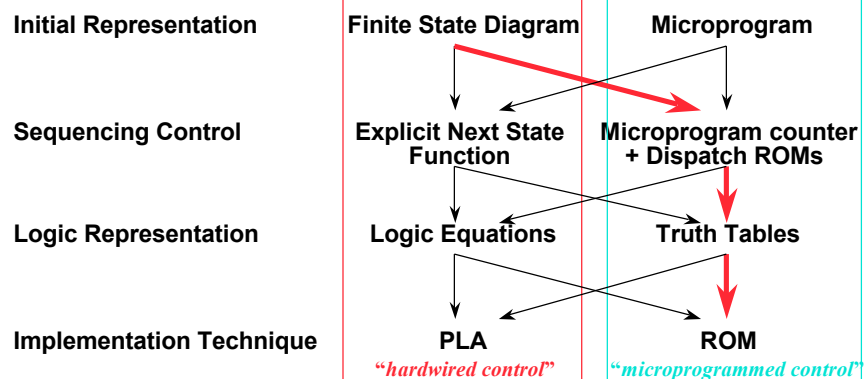Next Iteration: Using Microprogram for Representation



- ° ROM can be thought of as a sequence of control words
- ° Control word can be thought of as instruction: “microinstruction”
- ° Rather than program in binary, use assembly language

361 multicontroller.22

Microprogramming

- Control is the hard part of processor design
 - Datapath is fairly regular and well-organized
 - Memory is highly regular
 - Control is irregular and global

Microprogramming:


- A Particular Strategy for Implementing the Control Unit of a processor by "programming" at the level of register transfer operations

Microarchitecture:

- Logical structure and functional capabilities of the hardware as seen by the microprogrammer

361 multicontroller.23

Macroinstruction Interpretation

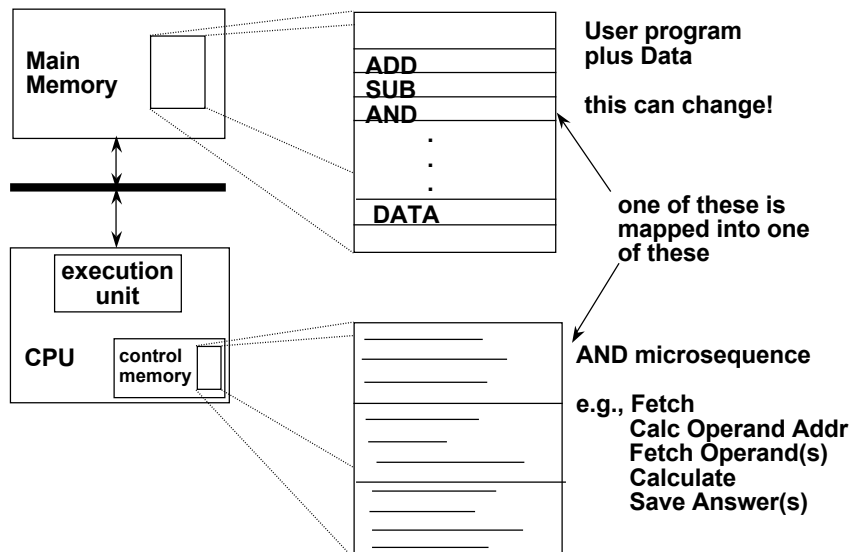

361 multicontroller.24


Microprogramming Pros and Cons

- Ease of design
- Flexibility
 - Easy to adapt to changes in organization, timing, technology
 - Can make changes late in design cycle, or even in the field
- Can implement very powerful instruction sets (just more control memory)
- Generality
 - Can implement multiple instruction sets on same machine.
 - Can tailor instruction set to application.
- Compatibility
 - Many organizations, same instruction set
- Costly to implement
- Slow

361 multicontroller.25

Summary: Multicycle Control

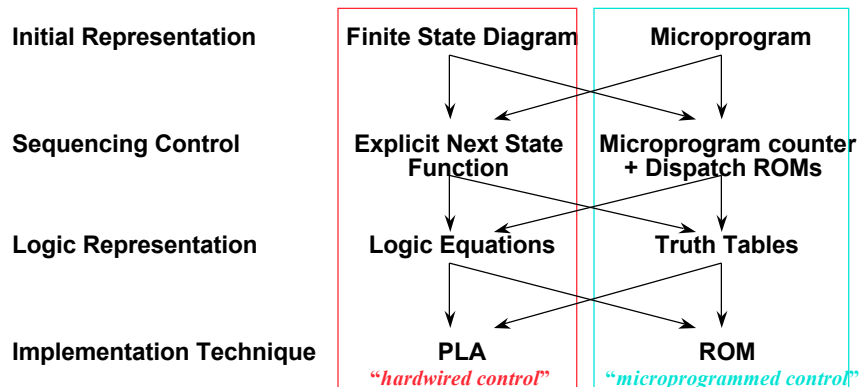- Microprogramming and hardwired control have many similarities, perhaps biggest difference is initial representation and ease of change of implementation, with ROM generally being easier than PLA



361 multicontroller.26